## Λογική Σχεδίαση

## Εργαστηριακή Άσκηση 4

Όνοματεπώνυμο: Πασχάλης Μοσχογιάννης

Αριθμός Μητρώου: 2114026

**A)** 

ΛΑ=Α "1"=πράσινο ΦΑΒ=ΥΑΒ ΛΒ=Β "0"=κόκκινο ΦCD=YCD

 $\Lambda C = C$  $\Lambda D = D$ 

 $\Lambda C = 1$  &&  $\Lambda D = 1$  &&  $\Lambda A = 0 \parallel \Lambda B = 0$   $\Lambda C = 1 \parallel \Lambda D = 1$  &&  $\Lambda A = 0$  &&  $\Lambda B = 0$ 

A	В	С	D	YAB	YCD
0	0	0	0	1	0
0	0	0	1	0	1
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	0	1	1	0
0	1	1	0	1	0
0	1	1	1	0	1
1	0	0	0	1	0
1	0	0	1	1	0
1	0	1	0	1	0
1	0	1	1	0	1
1	1	0	0	1	0
1	1	0	1	1	0
1	1	1	0	1	0
1	1	1	1	1	0

• YAB = A'B'C'D' + A'BC'D' + A'BCD' + A'BCD' + AB'C'D' + AB'C'D + ABCD' + AB


AB\CD	00	01	11	10
00	1	0	0	0
01	1	1	0	1
11	1	1	1	1
10		1	0	1

YAB=C'D'+AB+BC'+AC'+BCD'+ACD'


## YCD=A'B'C'D + A'B'CD' + A'B'CD + A'BCD + AB'CD

AB\CD	00	01	11	10
00	0	1	1	1
01	0	0		0
11	0	0	0	0
10	0	0	1	0

YCD=A'B'D + A'B'C + A'CD + B'CD

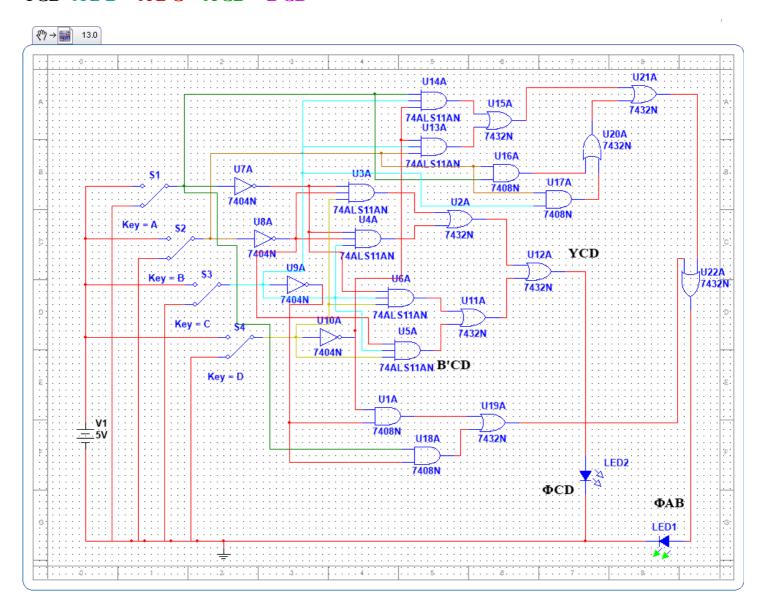

A	В	Z=A'B + AB'	K=AB
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

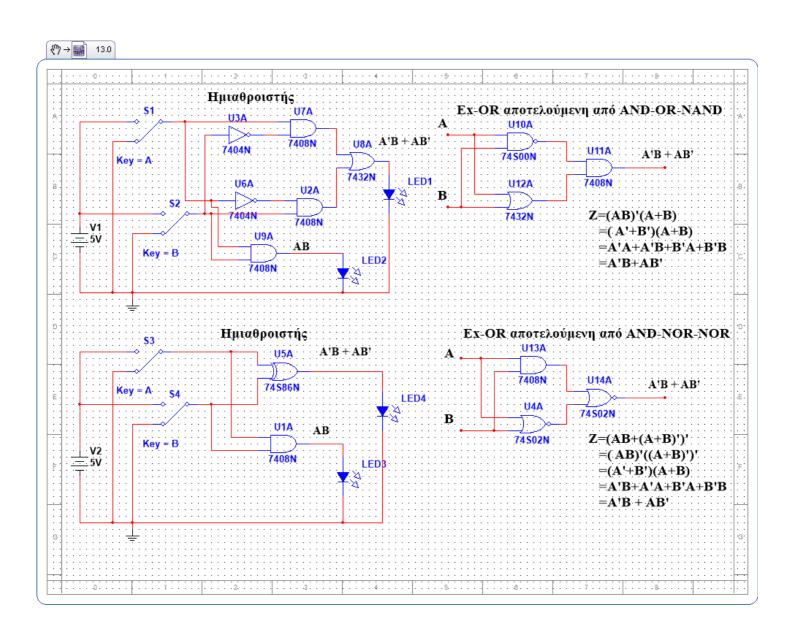



A	В	K	S	С
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- S=A'B'K + A'BK' + AB'K' + ABK=(A+B+K)(AB+BK+AK)' + ABK
- C=A'BK + AB'K + ABK' + ABK

A∖BK	00	01	11	10
0	0	0	1	0
1	0	1	1	1


• C=AK+AB+BK

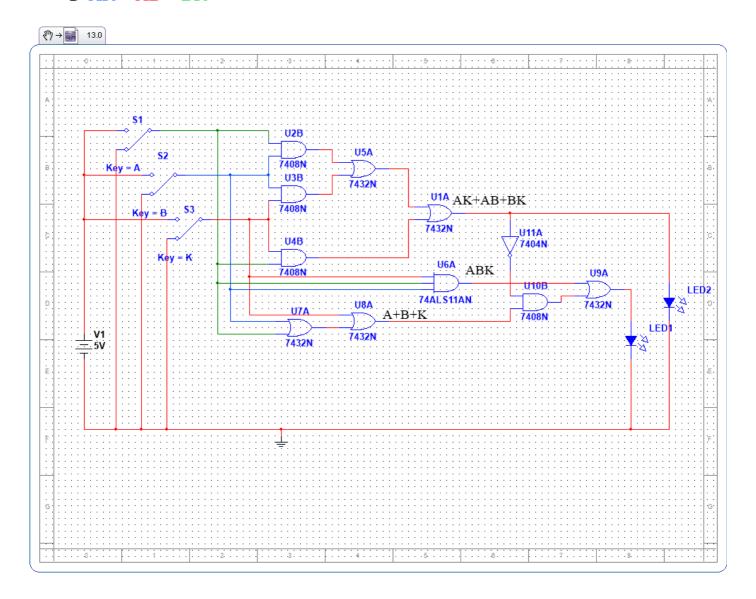

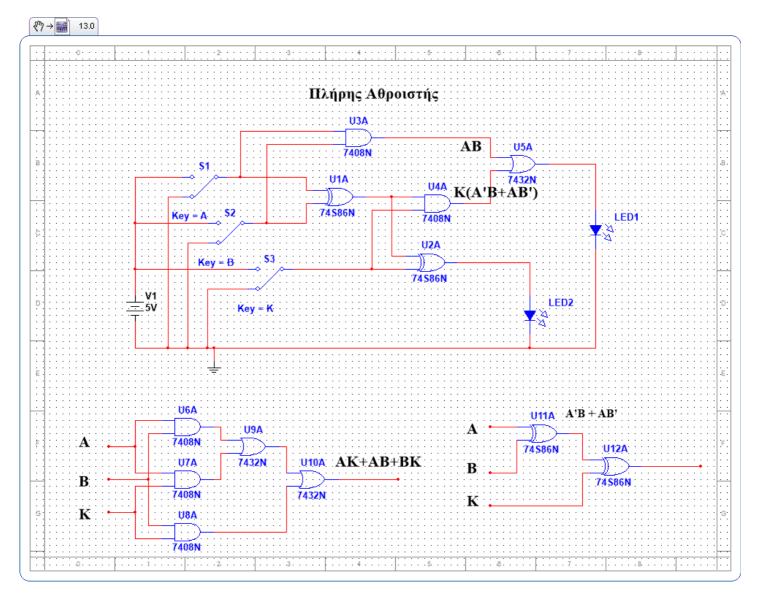

 $N=2 \mod 3 => N=2$ 

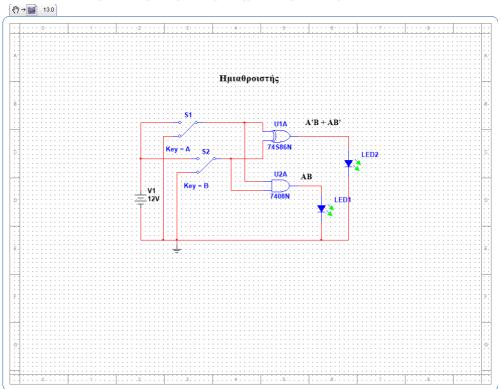Άρα προκύπτει ένας 2bit αθροιστής δηλαδή ο ημιααθροιστής




Γ) B=026 mod 16=10

D 020 mod 10 10				
a	b	С	d	y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

## Y=ab'cd + abc'd' + abc'd + abcd' + abcd

ab\cd	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	0	0	1	0

Y=ab + acd

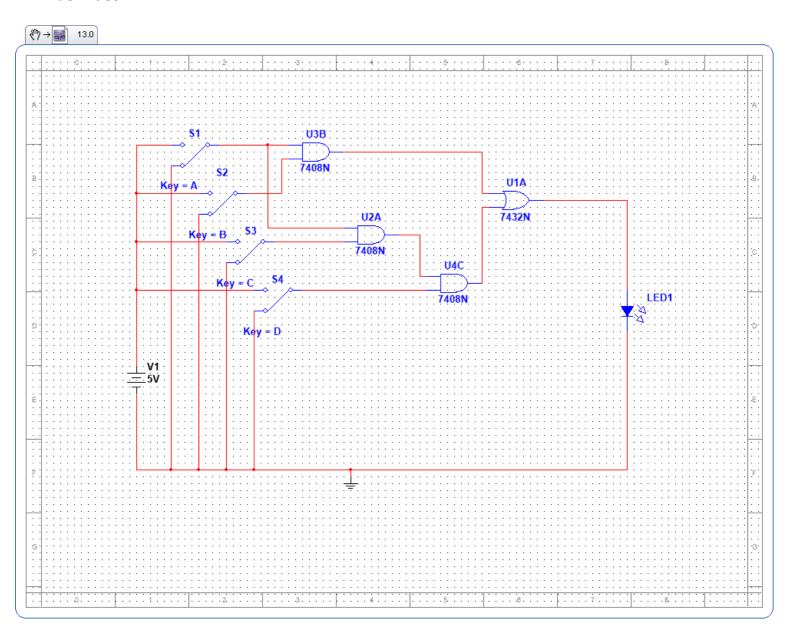

 $\Delta$ ) N=2 mod 3 => N=2

Πίνακας Αληθείας Συγκριτή Ισότητας 2 bits					
A	В	С	D	X=Y	
0	0	0	0	1	
0	0	0	1	0	
0	0	1	0	0	
0	0	1	1	0	
0	1	0	0	0	
0	1	0	1	1	
0	1	1	0	0	
0	1	1	1	0	
1	0	0	0	0	
1	0	0	1	0	
1	0	1	0	1	
1	0	1	1	0	
1	1	0	0	0	
1	1	0	1	0	
1	1	1	0	0	
1	1	1	1	1	

AB\CD	00	01	11	10
00	1	0	0	0
01	0	1	0	0
11	0	0	1	0
10	0	0	0	1

 $\overline{Y=(A\oplus C)(B\oplus D)}$ 

